

Lab3 - FSMs with Verilog

Digital Circuit and Systems
Department of Electronics Engineering
National Chiao Tung University

Data Preparation

Extract test data from TA's directory:

```
% tar zxvf ~DCSta01/DCS_LAB3.tar
```



Problem Description

Finite State Machine

Divide a sequential circuit operation into finite number of states.

A state machine controller can output results depending on the input signal, control signal and states.

 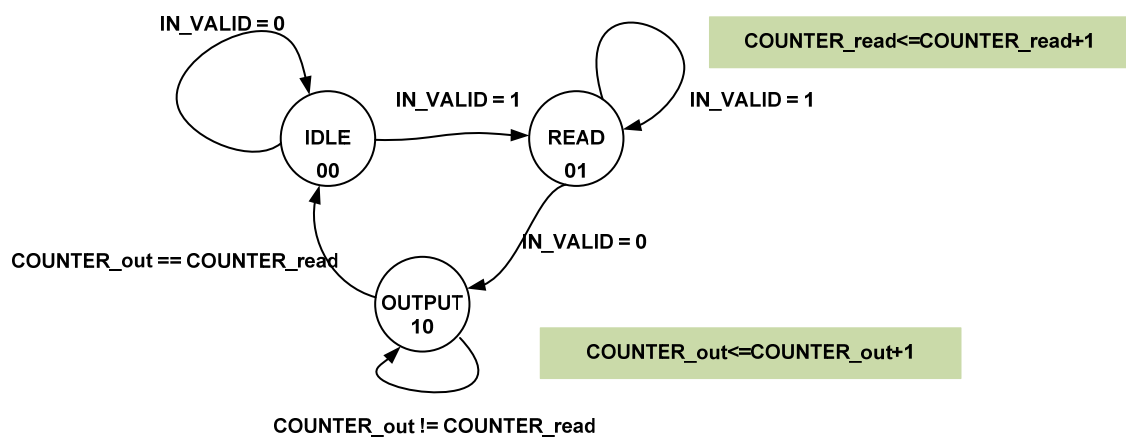As different input or control signal changes, the state machine will take a proper state transition.



```

always @ (posedge CLK)
    if(RST)
        CURRENT_STATE<=2'b00;
    else
        CURRENT_STATE<=NEXT_STATE;

always @*
    case(CURRENT_STATE)
        2'b00:
            if(IN_VALID==1'b1)
                NEXT_STATE<=2'b01;
            else
                NEXT_STATE<=CURRENT_STATE;
        2'b01:
            if(IN_VALID==1'b0)
                NEXT_STATE<=2'b10;
            else
                NEXT_STATE<=CURRENT_STATE;
        2'b10:
            if(COUNTER_out==COUNTER_read)
                NEXT_STATE<=2'b00;
            else
                NEXT_STATE<=CURRENT_STATE;
    endcase

```

Given Input

Input: 1-bit CLK, RST, IN_VALID

3-bits INPUT

Output: 3-bits OUT.

1-bit OUT_VALID

Synchronous active high reset is used, and only once

輸入為 3bit 的 INPUT, 當 IN_VALID = 1 時, 要去讀取 INPUT 的值, IN_VALID 可能維持 1~5 個 cycle(等同於可能輸入 1~5 個值). 此次 LAB 題目就為利用 FSM 去讀取動態的輸入值, 存取後在最後輸出. 輸出時 OUT_VALID 要 = 1, OUT 就為輸出值.

hint: 使用 register 來存值, 使用 counter 來算輸入值的個數.

Execution of your program

Your program will only be executed with the following command. If your program fails to execute the following command, you will receive no credit for this lab.

%ncverilog -f Run.f